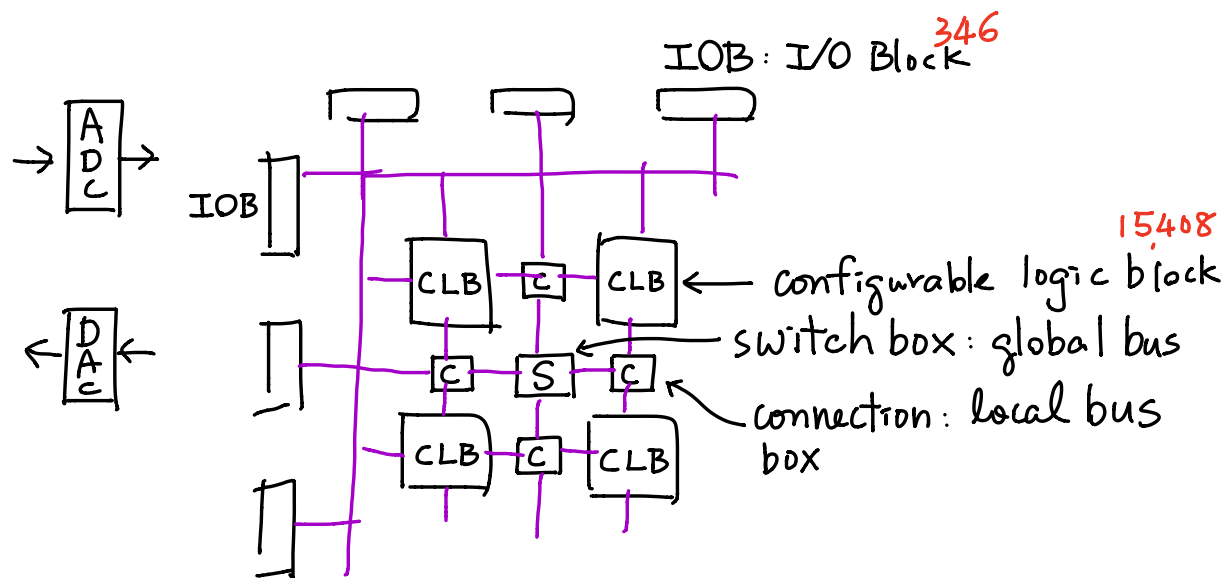


## FPGA field programmable gate array

Are you tired of

1. Spending a lot of time building circuit?
2. Throw away circuits built incorrectly?
3. Cannot copy and paste circuits?
4. Worry the circuit will smoke when you turn it on?
5. Waste material when the circuit is no longer useful?

FPGA comes to your rescue.




Other stuffs: CLK, Power supply, USB, SD card,

Expansion slots. Flash/RAM


On/off switch. LED display. ADC/DAC.

7 segment display

# Configurable Logic block CLB

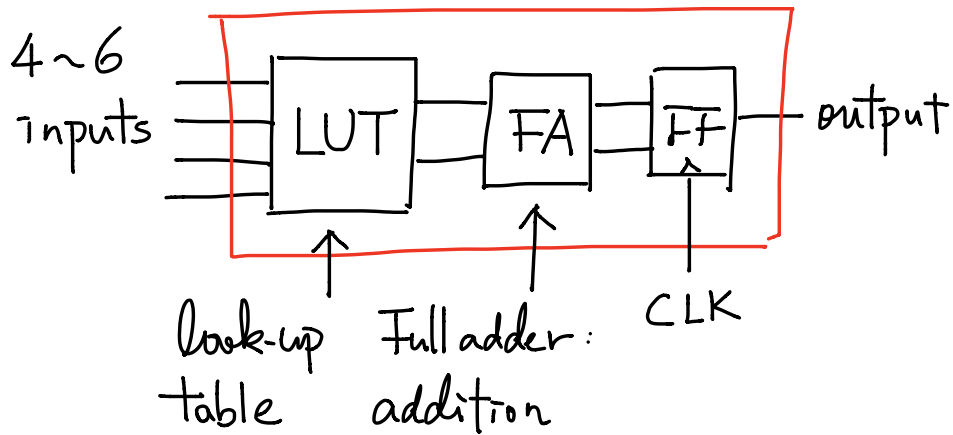


How do you build a look up table LUT?

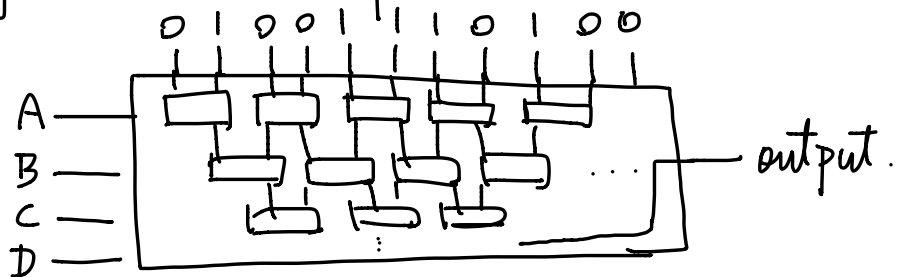

6 possible connections

Switch block:

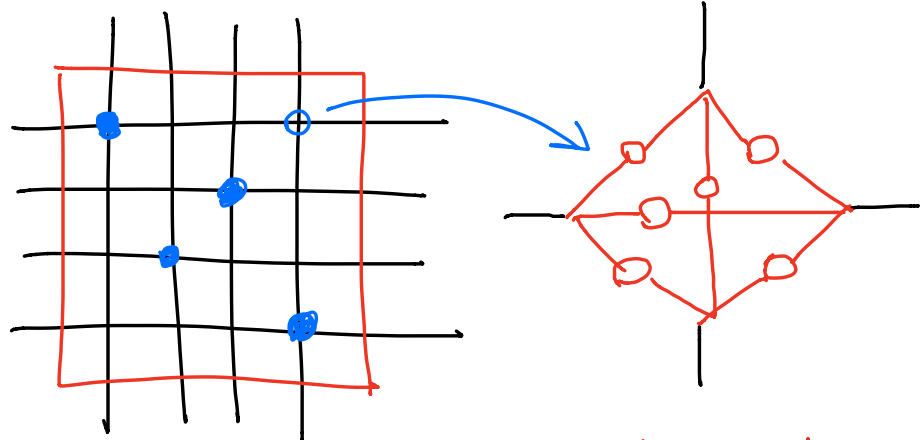

This is called routing.

$$\text{Symbol} = \begin{matrix} D \\ G \\ S \end{matrix}$$