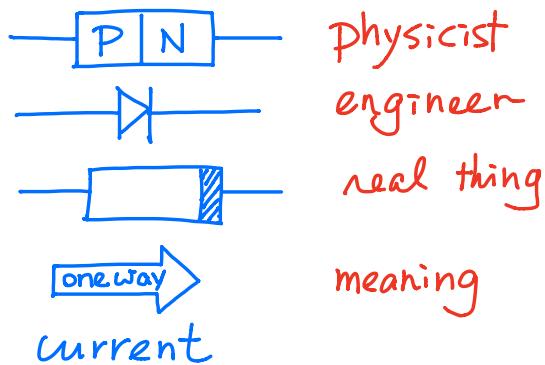


What is a diode?



Types of diodes:

generic diode limit voltage range

Zener diode: voltage reference (reverse bias mode)

Light emitting diode: emit light when forward biased

Shottkey diode: high speed generic diode


photodiode: convert photons into electrons.

laser diode: convert electric current into coherent light.


varistor: voltage limiter for power applications.

Electrical characteristic :

Ideal diode

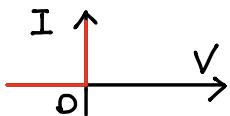


Measurement scheme.

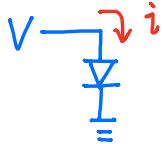


$V > 0$: short circuit $\approx -$

$V < 0$: open circuit $\approx \perp$

Real diode

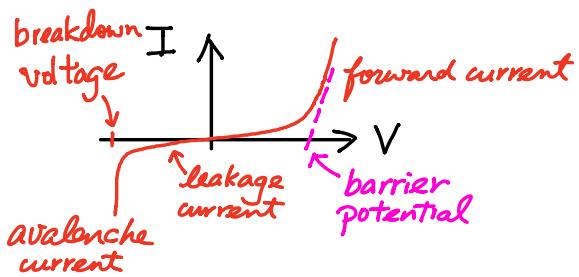

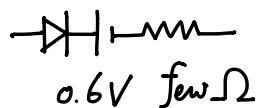Effective circuit in the forward direction:



* Other than Zener diodes designed to operate in the reverse-biased regime for regulation, other types of diodes can break down with strong reverse bias.

Working model :




$V > 0.6V$: short circuit with a diode drop.

$V < 0V$: open circuit

$V \ll -1V$: no-good. Can lead to damage.

Applications:

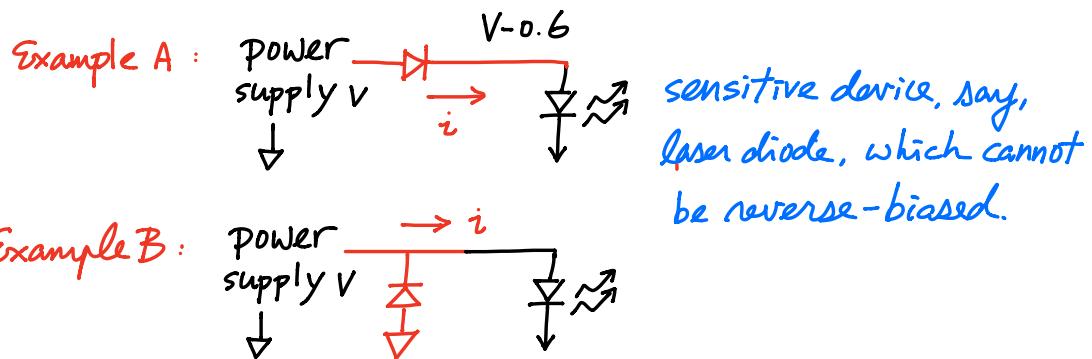1. Protection: diode prevents reverse current



What's the difference?

ExA: limits reverse current $I > -I_{reverse}$
ExB: limits reverse voltage $V > -0.6V$

2. Rectifier: convert AC signal into DC signal

