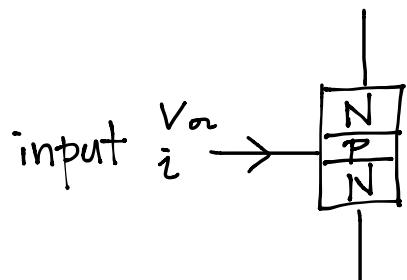


Transistor (transconductance resistor) is a three terminal device to switch or amplifier signals.





Idea:

Electronically control the main circuit

Voltage mode: high V : $R=0 \rightarrow \text{on}$
low V : $R=\infty \rightarrow \text{off}$

Current mode: small current induces big current.


When the transistor is on

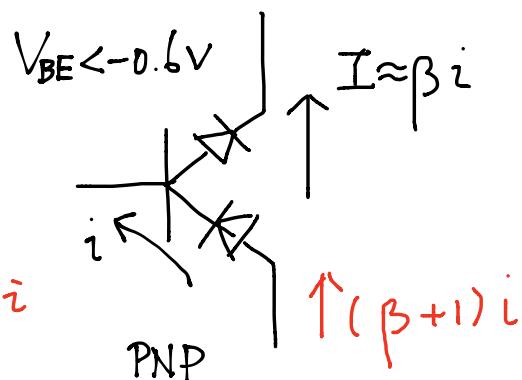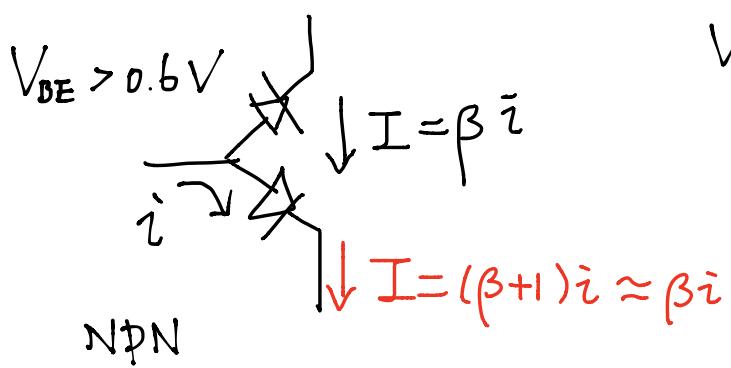

Rules for NPN transistor


1. Collector is more positive than Emitter.
2. Base-emitter and base-collector are effectively diodes.
3. $I_{\text{collector}} = \beta I_{\text{base}}$. Beta can be as high as 60-100
4. Constraints: I_{base} , $I_{\text{collector}}$ and V_{ce} should not be too high.
Typically $I_{\text{collector}} < 0.1\text{-}1 \text{ A}$ and $V_{\text{ce}} < 15\text{-}40 \text{ V}$.

Model of a NPN transistor:

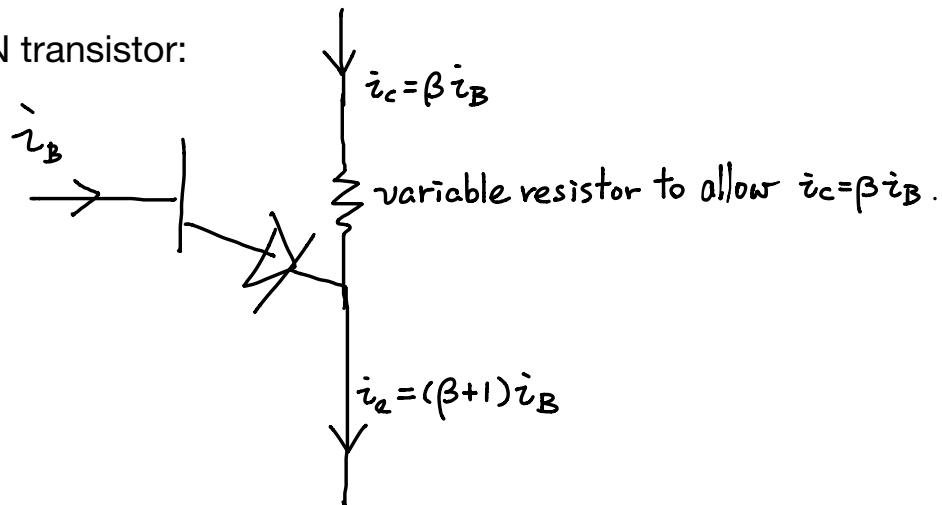


Applications:

1. Switch

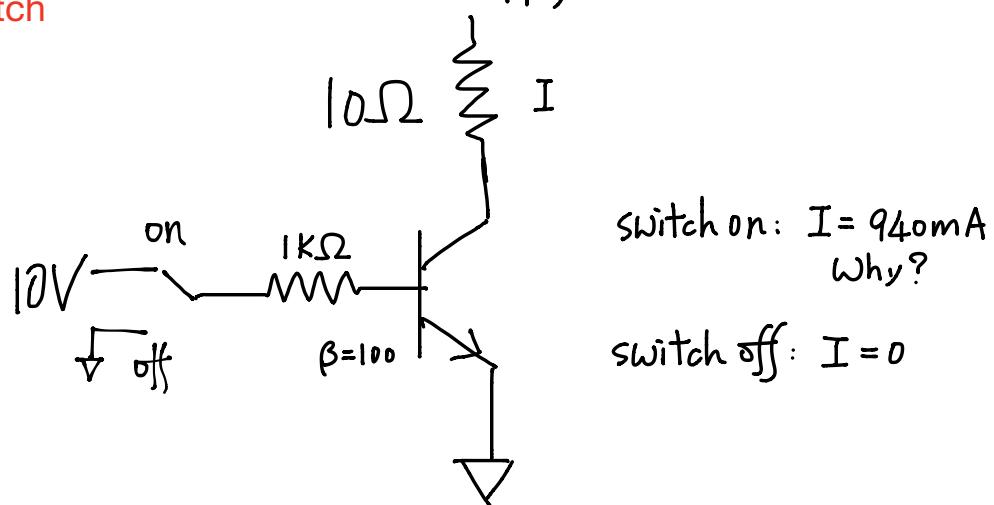

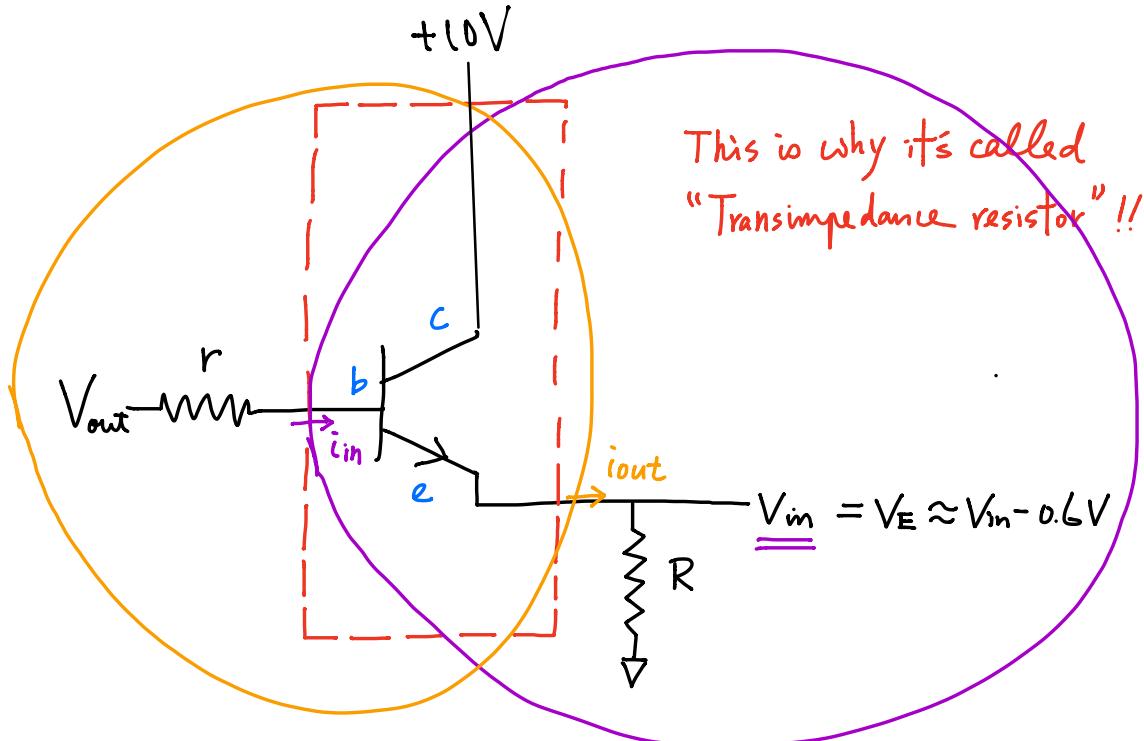Emitter follower: emitter follows the input (base), less one diode drop, with a factor of beta lower output impedance or higher input impedance:




Impedance change: (look at the purple circle)

input impedance:

$$\begin{aligned} Z_{in} &= \Delta V_{in} / \Delta I_{in} \\ &= \Delta i_{out} R / \Delta i_{in} \\ &= (\beta + 1) R \end{aligned}$$

Reminder:

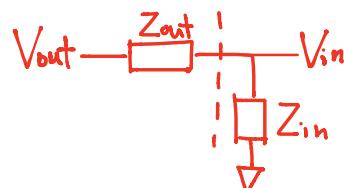

Input impedance improved by $(\beta + 1)$!!

Reminder: the higher the input impedance the better.

Output impedance : look at the orange circle


$$\begin{aligned} Z_{\text{out}} &= \Delta V_{\text{out}} / \Delta i_E = \Delta V_E / \Delta i_E \\ &= \Delta V_b / (\beta + 1) \Delta i_B \\ &= r / (\beta + 1) \end{aligned}$$

Output impedance reduced by $(\beta + 1)$.

A single transistor makes both input/output devices happier by a factor of $\beta + 1$.

Extension:


Darlington Pair:

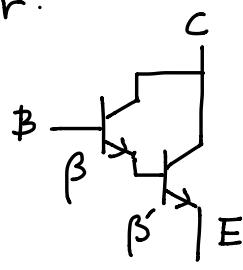

further improve current amplification to

$$\beta_{\text{eff}} = (1 + \beta)(1 + \beta')$$

Transistor as a current source

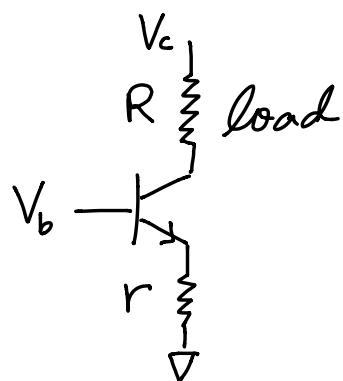

transistor on :


$$V_c = \beta i_b R + (\beta + 1) i_b r$$

$$\Rightarrow i_c = \beta i_b \approx V_c / (R + r)$$

$$\begin{aligned} V_b &> 0.6 + (\beta + 1) i_b r \\ &> 0.6 + V_c \frac{r}{R + r} \end{aligned}$$

Transistor off : $V < 0.6 + V_c \frac{r}{R + r}$

Transistor as an amplifier:

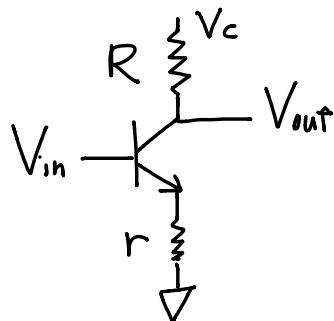

Working in the regime $i_c = \beta i_b$,
we have

$$\begin{aligned}V_{out} &= V_c - i_c R \\&\approx V_c - i_e R \\&= V_c - \frac{V_{in} - 0.6}{r} R\end{aligned}$$


What do we assume here?

AC gain

$$\begin{aligned}G_{AC} &= \frac{\delta V_{out}}{\delta V_{in}} \\&= -\frac{R}{r}\end{aligned}$$

Example: design a transistor amplifier with $G_{AC} = 10$
 for a weak signal with a power supply 10V.

Step 1: make sure it can amplify.

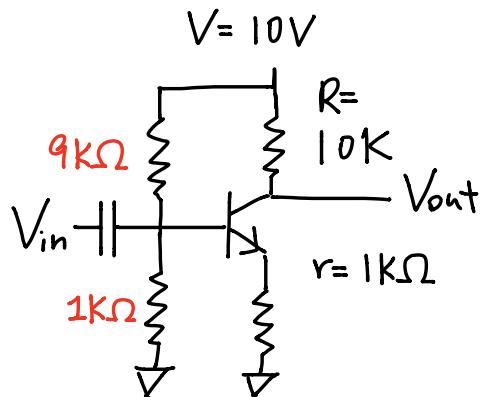

$$\begin{aligned}\delta V_{out} &= -R \delta i_c \\ &= -R \delta i_e \\ &= -R \delta V_{in}/r \\ &= -\frac{R}{r} \delta V_{in} = -10 \delta V_{in}\end{aligned}$$

Step 2: check the assumptions
 OK

$$\delta i_c \approx \delta i_e \text{ fine}$$

$$\delta i_e = \delta V_{in}/r \text{ assumes what?}$$

- A. transistor is on $V_{be} = V_{in} - i_e r > 0.6 \Rightarrow V_{in} > 0.6 + i_e r$
- B. V_{in} cannot be too large: transistor can only be completely on.
 $\Rightarrow i_e < \frac{V}{R+r} = 9 \text{ mA}$

$$\Rightarrow V_{in} = 0.6 + i_e r < 0.6 + \frac{r}{R+r} V$$


$$\text{Together we have } 0.6 < V < 0.6 + \frac{1}{11} * 10 \approx 1.5$$

So we should bias V_{in} by, say, 1V, and thus

$$i_e = 0.4/1k = 0.4 \text{ mA}, V_{out} \text{ is biased by } 6V$$

$$V_{out} = 6 - 10 V_{in} \text{ } \cancel{\text{*}}$$

A complete Ac friendly circuit!

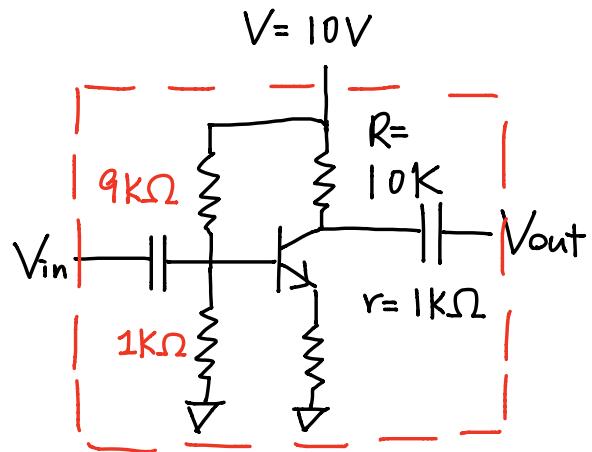

Our first non-trivial circuit!!