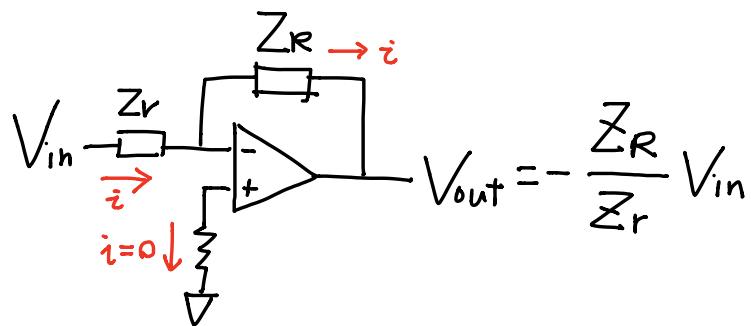


Op-amp Operational Amplifier

Goals of these 2 classes:

1. Golden rules.
2. How do op-amps work? Answer: feedback!!
3. How to do arbitrary signal processing?



Golden rules of an ideal op-amp:

1. $V_+ = V_-$


2. V_+ & V_- terminals do not source/drain current.


Step 1: $V_+ = V_- = 0$ (from both rules)

Step 2: $i_{in} = \frac{V_{in}}{Z_{in}} \Rightarrow V_{out} = -i Z_R = -\frac{Z_R}{Z_r} V_{in}$

$\Rightarrow G = -\frac{Z_R}{Z_r}$ 100 K

Example:

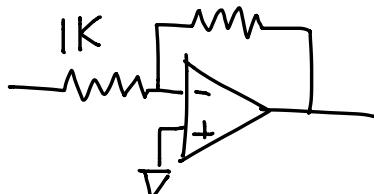

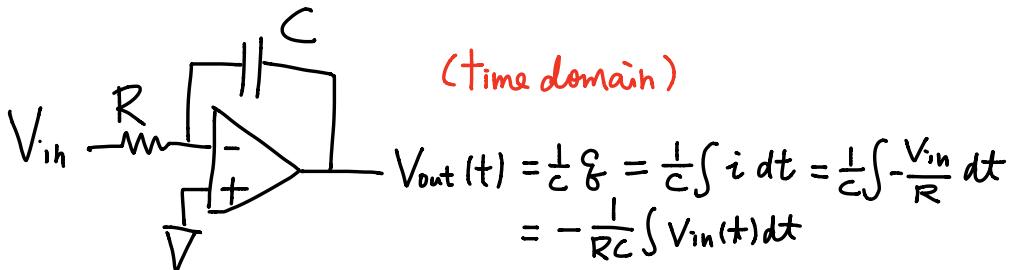

(freq domain)

$$V_{out} = -\frac{Z_R}{Z_r} V_{in} = -\frac{1}{iRC\omega} V_{in}$$

Prove 2 pictures are identical:

$$V_{in}(t) = V_{in} e^{i\omega t} \Rightarrow \int V_{in}(t) dt = \frac{1}{i\omega} V_{in} e^{i\omega t}$$

$$V_{out}(t) = V_{out} e^{i\omega t} \Rightarrow V_{out} e^{i\omega t} = -\frac{1}{RC} \frac{1}{i\omega} V_{in} e^{i\omega t}$$

identical as the freq domain result.

\Rightarrow Gain $G = -\frac{1}{i\omega RC}$ means an integer !!


$$y = A \int x(t) dt.$$

$$V_{out} = -\frac{1}{RC} \frac{1}{i\omega} V_{in}$$

Where is $i\omega$ coming from? $\partial_t f(t) = i\omega f(t)$, when f oscillates @


$$\Rightarrow i\omega = \partial_t \Rightarrow V_{out} = -\frac{1}{RC} \frac{1}{\partial_t} V_{in} ??$$

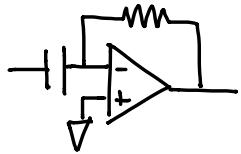on $V_{in} = -RC i\omega V_{out}$
 $= -RC \partial_t V_{out}$



$$G = -\frac{Z_R}{Z_r} = -\frac{R}{\frac{1}{i\omega C}} = i\omega RC$$

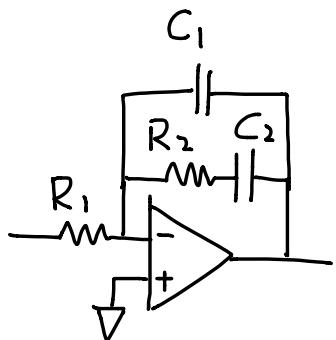
$V_{out} = i\omega RC V_{in} = RC \frac{d}{dt} V_{in} \Rightarrow \text{differentiator !!}$



$$\begin{aligned} G &= -\frac{1}{R_1} \left[\left(R_2 + \frac{1}{i\omega C_2} \right) \parallel \frac{1}{i\omega C_1} \right] \\ &= -\frac{1}{R_1} \frac{R_2 + \frac{1}{i\omega C_2}}{\left(R_2 + \frac{1}{i\omega C_2} + \frac{1}{i\omega C_1} \right) i\omega C_1} \\ &= -\frac{1}{R_1} \frac{1 + i\omega R_2 C_2}{i\omega (C_1 + C_2) - \omega^2 R_2 C_1 C_2} \end{aligned}$$

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


Summing amplifier

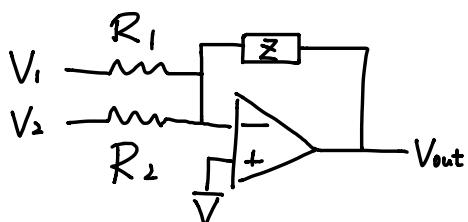

$$i = i_1 + i_2$$

$$\begin{aligned} \Rightarrow V_{out} &= -i Z \\ &= -Z \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \end{aligned}$$

Non-inverting amplifier

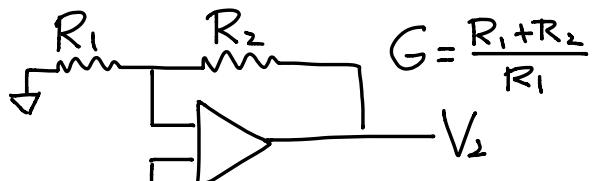

Difference amplifier

