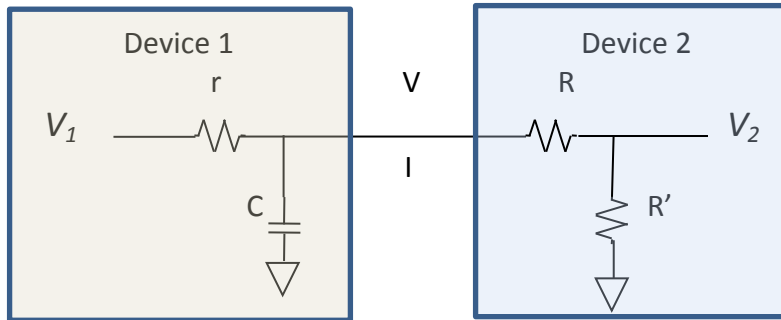


1. Impedance: resistors, capacitors, and inductors

(A) Device 1 delivers a signal to Device 2. Calculate the output impedance and input impedance as a function of the angular frequency ω .

(Hint: you may assume the actual output voltage and current are V and I . Thus output impedance is $Z_{out} = |dV/dI|$, expressed in terms of r and C . Input impedance is $Z_{in} = |dV/dI|$ expressed in terms of R and R' .)



Solution:


$$I = \frac{V_1 - V}{r} - \frac{V}{Z_c} \Rightarrow dI = -\left(\frac{1}{r} + \frac{1}{Z_c}\right) dV \Rightarrow Z_{out} = \left|\frac{dV}{dI}\right| = \left|\frac{rZ_c}{r + Z_c}\right| = \frac{r}{\sqrt{1 + \omega^2 r^2 C^2}}$$

$$V = I(R + R') \Rightarrow Z_{in} = \left|\frac{dV}{dI}\right| = R + R'$$

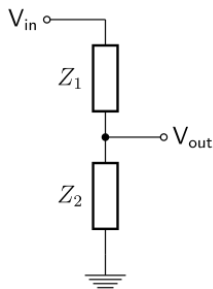(B) Bandblock: Design an *RLC* circuit between Device 1 and Device 2 such that only signal at a desired angular frequency ω_0 will be completely blocked.


Solution: $V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$. The simplest way to satisfy the required condition is $Z_1 = R$

And $Z_2(\omega_0) = i\omega_0 L + \frac{1}{i\omega_0 C} = 0$. Thus we can choose $LC = \frac{1}{\omega_0^2}$.



2. Transistors and amplifier

(A) Darlington pair:

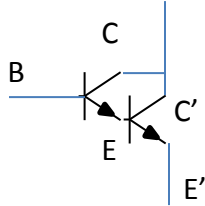


The above Darlington pair is made of 2 identical diodes with current amplification of $I_c = \beta I_B$ and $\beta=60$ is the amplification factor. Given a small base current $I_B = 1 \mu\text{A}$, determine the currents flowing through the collector terminals of each transistor I_C and $I_{C'}$.

Solution: $\beta \mu\text{A}$, $\beta(\beta+1) \mu\text{A}$

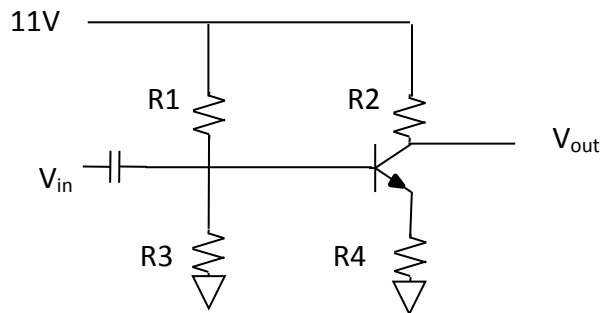(B) Transistor amplifier

You wish to amplify an AC signal V_{in} by a factor of 10. How would you choose R_1 , R_2 , R_3 and R_4 to accomplish this task.




Solution: $R_2/R_3=10$, $1.6 > 11 R_3/(R_1+R_3) > 0.6$.

(c) What is the maximum range of the input voltage V_{in} that the amplifier circuit works?

Solution: V_{out} can reach maximum of 11 V (transistor fully off) and minimum of 1V (transistor fully on) with an amplification of 10. Thus V_{in} can swing no more than 1V and thus $-0.5V < V_{in} < 0.5V$. (This happens when the R_1 and R_3 properly bias the input to $(0.6+1.6)/2 = 1.1$ V.)

3. Operational amplifiers

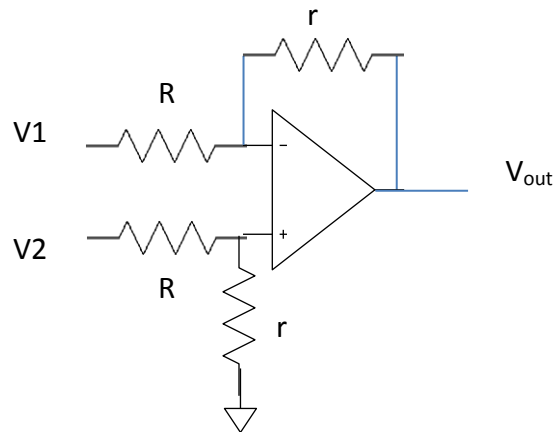(A) Calculate the gain $G=V_{out}/V_{in}$ of the following circuit, and explain its function.



Solution: Difference amplifier $V_{out} = (V_2 - V_1)(R/r)$.

(B) Design an Op-amp circuit to process two signals V_1 and V_2 such that $V_{out}(t) = dV_1(t)/dt + 2V_2(t)$.

Solution: We can write the desired formula as $V_{out} = 2 \left(V_2 - \frac{1}{2} \frac{dV_1}{dt} \right)$, which in frequency space is $V_{out} = 2 \left(V_2 - \frac{i\omega}{2} V_1 \right)$. Thus we can combine a differentiator on V_1 with a gain of $G = \frac{i\omega}{2}$ together with a difference amplifier as shown in (A) with a gain of $R/r=2$.

4. Feedback and car driving

You are driving on the highway at a constant speed, and your car drifts sideways from the center of the lane with an excursion x . Your goal is to keep the car centered or $x=0$. To reach this goal, you turn the steering wheel by θ .

For small excursion x , the transverse motion of the car can be described by

$$\frac{d^2x}{dt^2} = \alpha\theta + f(t),$$

where $f(t)$ is the random external force pushing the car sideways due to imperfect road condition, α is the steering sensitivity.

(A) Write the equation in the frequency domain.

(Hint: Use Fourier transform $y(t) = \int y(\omega)e^{-i\omega t}d\omega$, where $y(t)$ is the function in time domain, and $y(\omega)$ is the function in the frequency domain.)

Solution: $-\omega^2x(\omega) = \alpha\theta(\omega) + f(\omega)$

(B) If the external force is a white noise $f(\omega) = f_0 = \text{constant}$. Show that your car is very easily influenced by low frequency components of the external force if you do not control the steering wheel $\theta=0$.

Solution: We have $x(\omega) = -\frac{f_0}{\omega^2 - G}$. When $G=0$, x diverges at DC $\omega = 0$.

(C) One way to control your car is to turn the steering wheel in the opposite direction of the excursion $\theta = -Gx$, with a constant positive gain $G>0$. Such approach offers negative feedback, but shows that it still leads to diverging instability.

Solution: Given $G=\text{constant}$, x diverges at $\omega = \sqrt{G}$,

(D) Come up with a feedback strategy $\theta(\omega) = G(\omega)x(\omega)$ with a simple gain function $G(\omega)$ such that you can keep the car more stable at all frequencies $\omega \geq 0$.

(Hint: a car is considered more stable if the excursion x does not diverge at any frequency, and is smaller than that of an unsteered car at all frequencies.)

Solution: One simplest solution is to employ an integration gain $G = \frac{1}{i\omega C}$, which gives

$x = -\frac{f_0}{\omega^2 + \frac{i}{\omega C}}$. The oscillation amplitude $|x| = \frac{f_0^2 \omega C}{\sqrt{1 + C^2 \omega^6}}$ does not diverge at any frequency.