## Physics 143A: Honors Waves, Optics, and Heat


Spring Quarter 2025 Problem Set #2

Due: 11:59 pm, Tuesday, April 8. Please submit to Canvas.
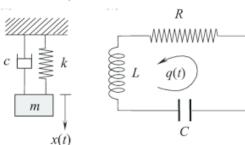
## 1. Simple harmonic oscillators in mechanics and electronics (10 points each)

Common oscillators in mechanics and electrodynamics are spring-mass system and RLC circuit, see figure on the right.

(Left) Consider a mass m is connected to a spring which exerts a force on the mass f=-kx(t), where k is the force constant. In addition, a damping force f=-cv(t) on the mass dissipates the energy and an external force F(t)



dissipates the energy and an external force F(t) can be applied to the mass.

(a) Show that the equation of motion on the mass is

$$mx''(t) + cx'(t) + kx(t) = F(t)$$

(b) Show that the intrinsic frequency of the oscillator is  $\omega_0=\sqrt{\frac{k}{m}}$ , and for the oscillator to show an underdamped oscillation, the damping coefficient should be  $c<2\sqrt{km}$  (Assume F(t)=0).

(Right) Voltages across a capacitor, resistor and inductor are  $V_c=\frac{q}{c}$ ,  $V_R=IR$ , and  $V_L=L\frac{dI}{dt}$ , where q is the charge across the capacitor, I=dQ/dt is the current flowing through the circuit, and the voltage drop over the wire loop is zero  $V_c+V_R+V_L=0$ .

- (c) Derive the differential equation of the charge q(t) and the current I(t) and show that they follow the equation of a damped harmonic oscillator, and the intrinsic frequency is  $\omega_0 = \frac{1}{\sqrt{IC}}$ .
- (d) Assume R = 0,  $q(0) = q_0$  and I(0) = 0, determine q(t) and I(t) of the circuit.

## 2. Quality factor of an oscillator

Crystal oscillators and atomic blocks are excellent time keepers and they operates under the principle of a driven harmonic oscillator with a low damping  $\gamma \ll \omega_0$ .

A driven RLC circuit equation is powered by a time-dependent voltage  $V(t)=V\sin\omega t$ , the equation is given by

$$Lq''(t) + Rq'(t) + \frac{1}{C}q(t) = V(t)$$

- (a) Derive the particular solution starting with the ansatz of  $q(t)=Qe^{i\omega t}$
- (b) The current through the circuit can be written as  $I(t) = I(\omega) \sin{(\omega t + \phi)}$ . Use any software to plot  $I(\omega)$ . Show that the profile  $I(\omega) \approx I_{max} \sqrt{L(\omega)}$  is described by the Lorentz distribution  $L(\omega) = \frac{1}{1 + \frac{(\omega \omega_0)^2}{\Gamma^2}}$ , when  $R/L \ll \omega_0$  and  $\omega \approx \omega_0$ . Determine the width of the

Lorentz distribution  $\Gamma$ , the maximum current  $I_{max}$ , and the ratio of the resonance frequency and the width  $Q=\frac{\omega_0}{\Gamma}$ , also called the Quality factor.

(Hint: for a bell-shaped distribution, width is typically defined as the range where the signal is above 50% of the maximum.)

- (c) Plot the phase shift  $\phi(\omega)$  for  $R/L=\omega_0/10$  and comment on the value of the phase shift when the driving force is far below resonance  $\omega\ll\omega_0$ , near the resonance  $\omega=\omega_0$  and well far above the resonance  $\omega\gg\omega_0$ .
- 3. Math Determine the eigenvalues and eigenvectors of the following matrices (5 points each)
  - (a)  $\binom{A B}{B A}$ (b)  $\binom{-1 \ 1 \ -1}{1 \ 0 \ 1}$
  - (c) A particle of mass 1 is moving in on the plane with potential energy  $V(x,y)=x^2+y^2-xy-6x$ . Determine the equilibrium position  $(x_0,y_0)$ , where the potential energy is at the minimum, and the two eigen-frequencies of the particle moving near the potential minimum.

(Hint: Taylor expand the potential near the minima. You may introduce a new coordinate  $u=x-x_0$ ,  $v=y-y_0$  and show that the equation of motion  $m\vec{r}''=-\nabla V(\vec{r})$  is given by

$$u'' = -2u + v$$
$$v'' = -2v + u.$$

You can then derive the eigenfrequencies.)

(d) Use the result in (c) and determine the eigen-frequencies of the particles moving near the minimum of the potential  $V(x,y)=e^{x^2+y^2-xy}$ .